

**Cairo University**  
**Faculty of Engineering**  
**Credit Hours System**



# **Computer Architecture (CMPN301)**

## **Report**

**Names:**

**Ali Said el Naggar 1180036**

**Abdallah Wael Marzouk 1180376**

**Mohamed Amr Afifi 1180062**

**Youssef Qadry Hashem 1180025**

## Instructions bit Details:

**Identifier bit (indicates if this Instruction is 16 or 32 bits (0 for 16, 1 for 32))**

### One Operand:

Bit 31-30: Operation Type  
Bit 29-27: Op Code for Function  
Bit 26-24: Register Address  
Bit 23-17: Not Used  
Bit 16: Identifier bit  
Bit 15-0: Not Used

Instruction	One Operand					
Instruction Bit	Bits 31-30	Bits 29-27	Bits 26-24	Bits 23-17	Bit 16	Bits 15-0
NOP	00	000	Not Used	Not Used	0	Not Used
SETC	00	001	Not Used	Not Used	0	Not Used
CLRC	00	010	Not Used	Not Used	0	Not Used
NOT Rdst	00	011	Rdst	Not Used	0	Not Used
INC Rdst	00	100	Rdst	Not Used	0	Not Used
DEC Rdst	00	101	Rdst	Not Used	0	Not Used
OUT Rdst	00	110	Rdst	Not Used	0	Not Used
IN Rdst	00	111	Rdst	Not Used	0	Not Used

## Two Operands:

Bit 31-30: Operation Type

Bit 29-27: Op Code for Function

Bit 26-24: Rdst Register Address

Bit 23-21: Rsrc Register Address / 23-19 Shift Amount

Bit 18-17: Not Used

Bit 16: Identifier bit

Bit 15-0: Immediate value for Add

Instruction	Two Operand						
Instruction Bit	Bits 31-30	Bits 29-27	Bits 26-24	Bits 23-21/23-19	Bits 18-17	Bit 16	Bits 15-0
Mov Rsrc, Rdst	01	000	Rdst	Rsc	Not Used	0	Not Used
ADD Rsrc, Rdst	01	001	Rdst	Rsc	Not Used	0	Not Used
IADD Rdst, Imm	01	010	Rdst	Not Used	Not Used	1	Immediate value
SUB Rsrc, Rdst	01	011	Rdst	Rsc	Not Used	0	Not Used
AND Rsrc, Rdst	01	100	Rdst	Rsc	Not Used	0	Not Used
OR Rsrc, Rdst	01	101	Rdst	Rsc	Not Used	0	Not Used
SHL Rsrc, Imm	01	110	Rdst	Not Used	Not Used	0	Not Used
SHR Rsrc, Imm	01	111	Rdst	Not Used	Not Used	0	Not Used

## Memory Operations:

Bit 31-30: Operation Type

Bit 29-27: Op Code for Function

Bit 26-24: Rdst Register Address

Bit 23-21: Rsrc Register Address

Bit 20-17: Not Used

Bit 16: Identifier bit

Bit 15-0: Immediate value for LDM to Register / Offset Address

Instruction	Memory Operand						
Instruction Bits	Bits 31-30	Bits 29-27	Bits 26-24	Bits 23-21	Bits 20-17	Bit 16	Bits 15-0
PUSH Rdst	10	000	Rdst	Not Used	Not Used	0	Not Used
POP Rdst	10	001	Rdst	Not Used	Not Used	0	Not Used
LDM Rdst, Imm	10	010	Rdst	Not Used	Not Used	1	Used
LDD Rdst, offset (Rsrc)	10	011	Rdst	Rsrc	Not Used	1	Used
STD Rsrc1, offset (Rsrc2)	10	100	Rdst	Rsrc	Not Used	1	Used

## Branch and Change of Control Operations:

Bit 31-30: Operation Type

Bit 29-27: Op Code for Function

Bit 26-24: Rdst Register Address

Bit 23-17: Not Used

Bit 16: Identifier bit

Bit 15-0: Not Used

Instruction	Branch and Change of Control Operations					
Instruction Bits	Bits 31-30	Bits 29-27	Bits 26-24	Bits 23-17	Bit 16	Bits 15-0
JZ Rdst	11	000	Rdst	Not Used	0	Not Used
JN Rdst	11	001	Rdst	Not Used	0	Not Used
JC Rdst	11	010	Rdst	Not Used	0	Not Used
JMP Rdst	11	011	Rdst	Not Used	0	Not Used
Call Rdst	11	100	Rdst	Not Used	0	Not Used
RET	11	101	Not Used	Not Used	0	Not Used

## Reset Signal:

When Reset = 0 , first mux of pc will make PC = 0 and output M[0]

## Control unit (23 bits)

- Receive first 5 bits from instruction to Decide which control signals should be sent

Signals are:

1- Memory Read enable (1 bit)

2 - Memory Write enable (1 bit)

3- Register Write enable (1 bit)

4- IF/D flush (1 bit)

5- ID/EX flush (1 bit)

6- Multiplexer Selector "Write Back Value" to choose between Data from memory or ALU result (1 bits)

7- Stack signal (5 bits) which are :

- SP enable (1 bit)
- SP Add or OLD (POP or push)
- SelectorSP (1 bit)
- SP or ALU result (Memory stage)
- PC + 1 or Read data 1 (Memory stage)

8- Signal for Forwarding unit for other operands ( 2 bits) one for each register

This signal controls multiplexers at ALU since Control unit has only 2 options: read data 1 or data 2 while forward unit has the other 2 options.

9- ALU operation Selector (4 bits)

10- Input and output Ports selector (2 bits)

- 1 bit for output port enable
- 1 bit for input port or ALU result

11- Jump Signals (3 bits)

- (1 bit) signal for flag enable
- (2 bits) jump signals for 4 jumps(zero,carry,negative,unconditional)

12 - Shift or immediate (1 bit)

13- PC selector (2 bits)


### Pipeline Registers details:

Register	Size	Input
IF/ID	98 bits	Input Port (32 bit) PC (32 bit) Instruction (32 bit) Enable (1 bit) Flush Signal (1 bit)
ID/EX	186 bits	Input Port (32 bit) PC (32 bit) Control Signal (18 bit) Read Data 1 (32 bit) Read Data 2 (32 bit) Extended Imm/Offset/ Shift (32 bit) Address for Rdst1 (3 bit) Address for Rsrc (3 bit) Enable (1 bit) Flush Signal (1 bit)
EX/MEM	110 bits	PC (32 bit) Control Signal (10 bit) Read Data 1 (32 bit) ALU Result (32 bit) Address for Rdst1 (3 bit) Enable (1 bit)
MEM/WE	102 bits	PC (32 bit) Control Signal (2 bit) Read Data 1 (32 bit) ALU Result (32 bit) Address for Rdst1 (3 bit) Enable (1 bit)

## Pipeline Hazards:
 
### Data Hazards:

Hazards due to register dependencies. When an instruction cannot be executed because it depends on an earlier one that doesn't hold the correct value yet.



### Control Hazards:

The control hazard faced in the design was when the branch instructions check for the flags - in the Execution stage- of the previous instruction, which isn't available. The Solution was to use Static Branch Prediction.

#### Static Branch Prediction (Predict not taken):

Automatically, the PC fetches the next instruction when the current one is in the decoding stage, it will remain until the execution stage of the current instruction.

After checking for the flags in the execution stage, if it's true, IF/ID and ID/EX buffers will flush and the PC will be changed to the new instruction. If it's false, the instruction will remain to the next stages

The unconditional jumps don't require checking for flags. Therefore, it doesn't wait for the execution and always sends the PC the address in the decode stage and the control unit adjusts the PC selector. So, unconditional jumps don't require prediction.

In RET, we will have to flush and stall the pipe 2 cycles till we get the PC value from the memory (*Stack*).

## Hazards Solutions:



### 1) Forwarding Unit:

The forwarding unit will check if the data (Rsrc) in this stage needs a data in (Rdst) from the previous stage(Read After Write)if the previous condition is true, the forwarding will take value from ALU or Memory to use it in the ALU, else the control unit will send a signal to the forwarding unit to choose another values in the ALU which are (Read data 1, Read data 2 or Immediate value)

### 2) Hazard Detection Unit:

Load Use Case,

If (ID/EX.MemRead ==1)

If (ID/EX.Rs2==IF/ID.Rs1) or (ID/EX.Rs2==IF/ID.Rs2)

{ PC Selector=0 Stall IF Stall ID }